



Ain Shams University
Faculty of Engineering
Computer and Systems Engineering Department

CSE 412: Digital Verification

4th Year CSE

2nd Semester 2021/2022

Assignment 2

Submitted by:

Sarah Mohamed Ahmed Ahmed

Code: 1700593

Section: 2

Submitted to:

Dr. Ayman Wahba

Github link: <https://github.com/Sarah-56/Digital-Verification/tree/main/latest>

Table of Contents

Design:	3
Interface:.....	3
Counter Module:	3
Test bench:	5
Assertion output:	7
Top module:	8
Output:	9

Design:

Interface:

```
interface Counter_Interface #(
    parameter COUNTER_SIZE = 4
)(
    input bit clk
);
    bit [1:0] ctrl, WHO;
    bit INIT, LOSER, WINNER, GAMEOVER, rst_l;
    bit [COUNTER_SIZE - 1:0] loadValue;

    clocking cb @(posedge clk);
        default input #0ns output #1ns;
        output rst_l, ctrl, INIT, loadValue;
        input WHO, LOSER, WINNER, GAMEOVER;
    endclocking

    modport dut(
        output GAMEOVER, WHO, LOSER, WINNER,
        input clk, rst_l, ctrl, INIT, loadValue
    );

    modport tb
    (
        clocking cb,
        output rst_l

    );
endinterface
```

Counter Module:

```
module counter #(
    parameter COUNTER_SIZE = 4          // number of bits in counter
)(
    Counter_Interface.dut sig
);
    /*******
        PARAMETERS
    *****/
    parameter cycle = 2;                // clock cycle = 2 msec.
    parameter whoValue = 2'b00;        //start value
    parameter upOne = 2'b00;           //00 count up by 1
    parameter upTwo = 2'b01;           //01 count up by 2
    parameter downOne = 2'b10;         //10 count down by 1
    parameter downTwo = 2'b11;         //11 count down by 2
    /*******
        REGISTERS & WIRES
    *****/
    reg LOSER;
    reg WINNER;
    reg GAMEOVER;
    reg [1:0] WHO;
    reg [1:0] ctrl;
    reg [COUNTER_SIZE - 1:0] m_counter;
    reg [COUNTER_SIZE - 1:0] loser_count;
    reg [COUNTER_SIZE - 1:0] win_count;
    wire [COUNTER_SIZE - 1:0] loadValue;
```

```

/*****
    ALWAYS BLOCK
    *****/
always @(posedge sig.clk) begin
    if (sig.INIT) begin
        m_counter = sig.loadValue;
        sig.WHO = whoValue;
        loser_count = 0;
        win_count = 0;
        sig.LOSER = 0;
        sig.WINNER = 0;
        sig.GAMEOVER = 0;
    end
    else begin
        /*****
            SYNCHRONOUS RESET
            *****/
        if (sig.rst_1 || sig.GAMEOVER) begin
            m_counter <= 4'b0000;
            sig.LOSER <= 0;
            sig.WINNER <= 0;
            sig.WHO <= 2'b00;
            loser_count <= 0;
            win_count <= 0;
            sig.GAMEOVER <= 0;
        end
        /*****
            INITIALIZATION
            *****/
        else if (sig.INIT) begin
            m_counter <= sig.loadValue;
            loser_count <= 0;
            win_count <= 0;
            sig.WHO <= 2'b00;
            sig.WINNER <= 0;
            sig.LOSER <= 0;
            sig.GAMEOVER <= 0;
        end
        else begin
            case (sig.ctrl)
                upOne: m_counter <= m_counter + 1;
                upTwo: m_counter <= m_counter + 2;
                downOne: m_counter <= m_counter - 1;
                downTwo: m_counter <= m_counter - 2;
            endcase
            /*****
                set LOSER signal to 1 for 1 clock cycle then clear it and increase
                loser counter by 1 if counter reaches 0
                *****/
            if(m_counter == 0) begin
                sig.LOSER <= 1;
                sig.WINNER <= 0;
                loser_count = loser_count + 1;
            end
            /*****
                set WINNER signal to 1 for 1 clock cycle then clear
                it and increase
                winner counter by 1 if counter reaches 15
                *****/

```

```

        else if(m_counter == 15) begin
            sig.WINNER <= 1;
            sig.LOSER <= 0;
            win_count = win_count + 1;
        end
        else begin
            sig.LOSER <= 0;
            sig.WINNER <= 0;
        end
        // raise gameover signal if loser or winner counter reaches 15
        if(loser_count == 15 || win_count == 15) begin
            sig.GAMEOVER <= 1;
            if(loser_count == 15) sig.WHO <= 2'b01;
            else sig.WHO <= 2'b10;
        end
    end
end
endmodule

```

Test bench:

```

program tb_counter(Counter_Interface.tb sig);
    /*******
        PARAMETERS
        *****/
    parameter cycle = 2;
    parameter COUNTER_SIZE = 4;
    /*******
        INITIAL BLOCK
        *****/
    initial begin
        sig.cb.loadValue <= 4'b0000;
        sig.cb.ctrl <= 2'b00;
        sig.cb.rst_l <= 0;
        sig.cb.INIT <= 1;
        for (int ctrl_c = 0; ctrl_c <= 3; ctrl_c = ctrl_c + 1) begin
            for(int loadValue_c = 0; loadValue_c < 3; loadValue_c = loadValue_c + 1)
begin
                assertion_1: assert (sig.cb.WINNER == 0)
                    $display("WINNER = %d asserted correctly", sig.cb.WINNER);
                else
                    $fatal("WINNER = %d not asserted correctly", sig.cb.WINNER);
                sig.cb.ctrl <= ctrl_c;
                if(loadValue_c == 2) sig.cb.loadValue <= {COUNTER_SIZE{1'b1}};
                else sig.cb.loadValue <= loadValue_c;
                sig.cb.INIT <= 0;
                #2
                sig.cb.rst_l <= 0;
                #2
                sig.cb.INIT <= 1;
                #1
                sig.cb.INIT <= 0;
                #481
                sig.cb.rst_l <= 1;
            end
        end
    end
end
    /*******
        Assign BLOCK
        *****/

```

```

assign WHO = sig.cb.WHO;
assign LOSER = sig.cb.LOSER;
assign WINNER = sig.cb.WINNER;
assign GAMEOVER = sig.cb.GAMEOVER;
/*****
    Properties
    *****/
property signals_cleared;
    @(sig.cb) disable iff(!($fell(sig.rst_1) )) (WHO ==0 || LOSER == 0 ||
        GAMEOVER == 0 || WINNER ==0);
endproperty

property winner;
    @(sig.cb)
        if($fell(sig.rst_1)) ##[100:200] GAMEOVER ==1;
endproperty

/*****
    Assertions
    *****/
assert_winner: assert property(winner)$display("[%0t] ---- Assertion GameOver
passed", $time);
assert_signals_cleared: assert property (signals_cleared) $display("[%0t] ----
Assertion Reseting_signals passed", $time);
endprogram

```

Assertion output:

```
WINNER = 0 asserted correctly
WINNER = 0 asserted correctly
[490] ----- Assertion Reseting_signals passed
"testbench.sv", 65: top.t0.assert_winner: started at 490ns failed at 890ns
      Offending '(GAMEOVER == 1)'
WINNER = 0 asserted correctly
[976] ----- Assertion Reseting_signals passed
"testbench.sv", 65: top.t0.assert_winner: started at 976ns failed at 1376ns
      Offending '(GAMEOVER == 1)'
WINNER = 0 asserted correctly
[1462] ----- Assertion Reseting_signals passed
[1692] ----- Assertion GameOver passed
WINNER = 0 asserted correctly
[1948] ----- Assertion Reseting_signals passed
[2192] ----- Assertion GameOver passed
WINNER = 0 asserted correctly
[2434] ----- Assertion Reseting_signals passed
[2664] ----- Assertion GameOver passed
WINNER = 0 asserted correctly
[2920] ----- Assertion Reseting_signals passed
"testbench.sv", 65: top.t0.assert_winner: started at 2920ns failed at 3320ns
      Offending '(GAMEOVER == 1)'
WINNER = 0 asserted correctly
[3406] ----- Assertion Reseting_signals passed
"testbench.sv", 65: top.t0.assert_winner: started at 3406ns failed at 3806ns
      Offending '(GAMEOVER == 1)'
WINNER = 0 asserted correctly
[3892] ----- Assertion Reseting_signals passed
"testbench.sv", 65: top.t0.assert_winner: started at 3892ns failed at 4292ns
```

```

    Offending '(GAMEOVER == 1)'
WINNER = 0 asserted correctly
[3406] ----- Assertion Reseting_signals passed
"testbench.sv", 65: top.t0.assert_winner: started at 3406ns failed at 3806ns
    Offending '(GAMEOVER == 1)'
WINNER = 0 asserted correctly
[3892] ----- Assertion Reseting_signals passed
"testbench.sv", 65: top.t0.assert_winner: started at 3892ns failed at 4292ns
    Offending '(GAMEOVER == 1)'
WINNER = 0 asserted correctly
[4378] ----- Assertion Reseting_signals passed
[4608] ----- Assertion GameOver passed
WINNER = 0 asserted correctly
[4864] ----- Assertion Reseting_signals passed
[5096] ----- Assertion GameOver passed
WINNER = 0 asserted correctly
[5350] ----- Assertion Reseting_signals passed
[5580] ----- Assertion GameOver passed
$finish at simulation time                    5832

```

Top module:

```

module top (output bit clk);
    initial clk = 1;
    initial forever #1 clk = ~clk;
    Counter_Interface iface(clk);
    tb_counter t0(iface.tb);
    counter G0(iface.dut);
    /*****
        DUMP VARIABLES
        *****/
    initial begin
        $dumpfile("wave.vcd");
        $dumpvars;
    end
endmodule

```


Output:

Control signal = 2'b00 (count up by 1)

Load value = 4'b0000

 


Figure 1

 


Figure 3

 


Figure 4

Control signal = 2'b00 (count up by 1)

Load value = 4'b0001

 


Figure 5

 


Figure 6

 


Figure 7

Control signal = 2'b00 (count up by 1)

Load value = 4'b1111

 


Figure 8

Control signal = 2'b00 (count up by 1)

Load value = 4'b1111

 


Figure 9

Control signal = 2'b01 (count up by 2)
Load value = 4'b0000

 


Figure 10

Control signal = 2'b01 (count up by 2)
Load value = 4'b0000

 


Figure 11

 


Figure 12

Control signal = 2'b01 (count up by 2)
Load value = 4'b0001

 


Figure 13

 


Figure 14

 


Figure 15

Control signal = 2'b01 (count up by 2)

Load value = 4'b1111

 


Figure 16

 


Figure 17

Control signal = 2'b10 (count down by 1)
Load value = 4'b0000

 


Figure 18

 


Figure 19

 


Figure 20

Control signal = 2'b10 (count down by 1)
Load value = 4'b0001

 


Figure 21

 


Figure 22

Control signal = 2'b10 (count down by 1)
Load value = 4'b1111

 


Figure 23

Control signal = 2'b11 (count down by 2)
Load value = 4'b0000

 


Figure 24

 


Figure 25

 


Figure 26

Control signal = 2'b11 (count down by 2)
 Load value = 4'b0001

 


Figure 27

Control signal = 2'b11 (count down by 21)
 Load value = 4'b1111

 


Figure 28